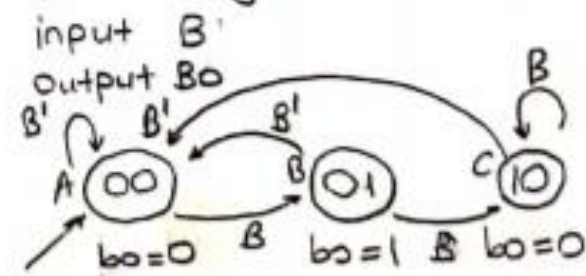



State Diagrams :



Truth Table


	s1	s0	B	n1	n0	B ₀
A	0	0	0	0	0	0
	0	0	1	0	1	0
B	0	1	0	0	0	1
	0	1	1	1	0	1
C	1	0	0	0	0	0
	1	0	1	1	0	0
Unused	1	1	0	0	0	0
	1	1	1	0	0	0
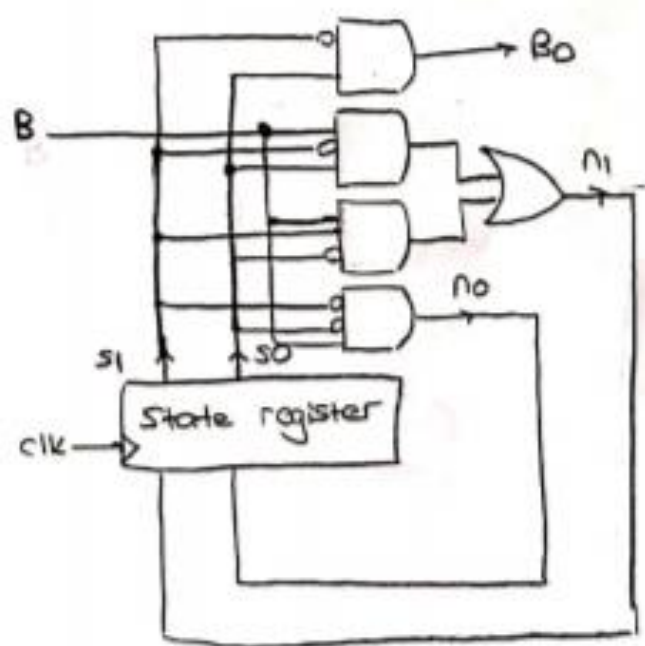
$$\begin{aligned}
 n1 &= s1's0B + s1s0'B \\
 n0 &= s1's0'B \\
 B_0 &= s1's0B + s1's0B' \\
 &= s1's0
 \end{aligned}$$



This diagram helps us to convert button press to single cycle duration, regardless of length of time that button was actually pressed


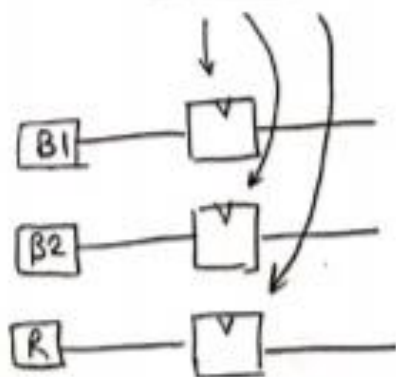
With help of this, in our game, when a player holds the button, cycle just one time will be 1




Main Game

Inputs : $B1, B2, R$

Outputs : $L0, L1, L2, L3, L4, L5, L6$

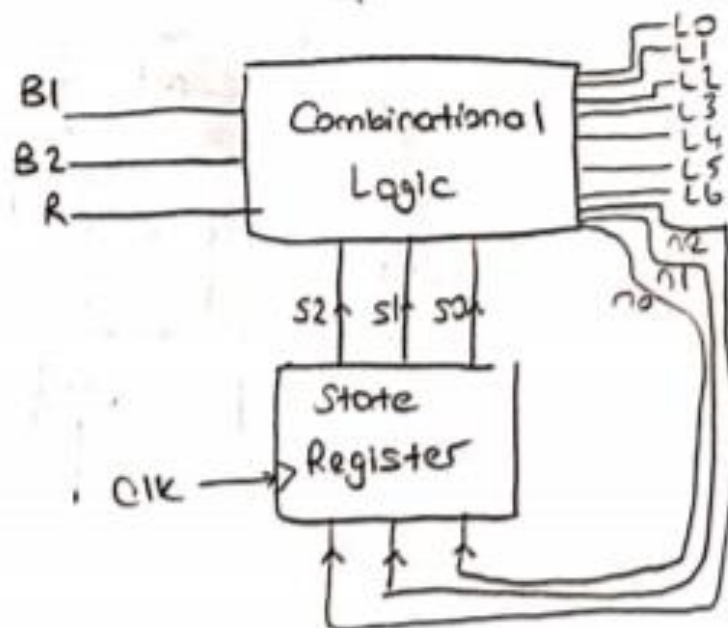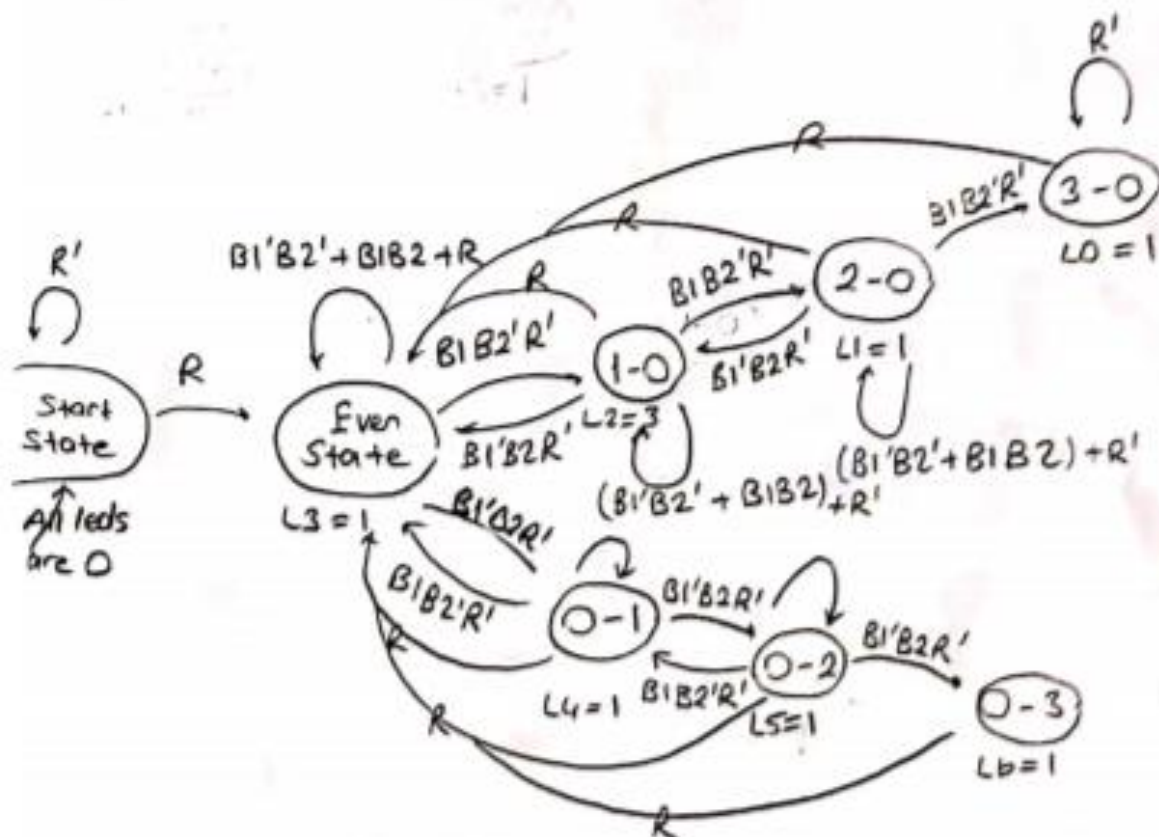

$$B1 \text{ XOR } B2 = A$$

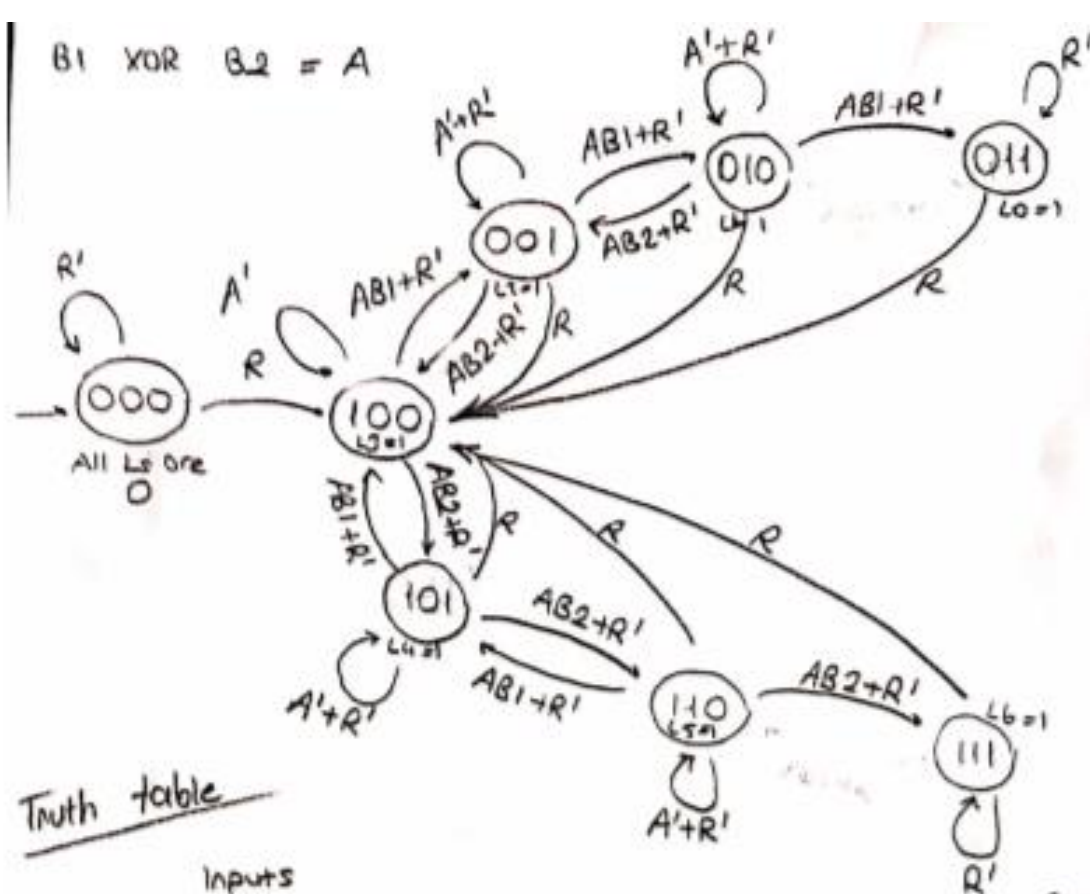

Truth table

Inputs

Outputs

s2	s1	s0	B1	B2	R	n2	n1	n0	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	1	1	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	1	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	1	0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	1	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	0	1	1	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	1	1	1	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0
0	0	1	1	0	1	1	0	0	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	1	1	1	0	0	0	0	0	0	0	0	0

Start State

1-0 State

S2	S1	S0	B1	B2	R	n2	n1	n0	L0	L1	L2	L3	L4	L5	L6	
0	1	0	0	0	0	0	1	0	0	1	0	0	0	0	0	2-0 State
0	1	0	0	0	1	1	0	0	0	1	0	0	0	0	0	
0	1	0	0	1	0	0	0	1	0	1	0	0	0	0	0	
0	1	0	0	1	1	1	0	0	0	1	0	0	0	0	0	
0	1	0	1	0	0	0	1	1	0	1	0	0	0	0	0	
0	1	0	1	0	1	1	0	0	0	1	0	0	0	0	0	
0	1	0	1	1	0	0	1	0	0	1	0	0	0	0	0	
0	1	0	1	1	1	1	0	0	0	1	0	0	0	0	0	

0	1	1	0	0	0	0	1	1	1	0	0	0	0	0	0	3-0 State
0	1	1	0	0	1	1	0	0	1	0	0	0	0	0	0	
0	1	1	0	1	0	0	1	1	1	0	0	0	0	0	0	
0	1	1	0	1	1	1	0	0	1	0	0	0	0	0	0	
0	1	1	1	0	0	0	1	1	1	0	0	0	0	0	0	
0	1	1	1	0	1	1	0	0	1	0	0	0	0	0	0	
0	1	1	1	1	0	0	1	1	1	0	0	0	0	0	0	
0	1	1	1	1	1	1	0	0	1	0	0	0	0	0	0	

1	0	0	0	0	0	1	0	0	0	0	0	1	0	0	0	Even state
1	0	0	0	0	1	1	0	0	0	0	0	1	0	0	0	
1	0	0	0	1	0	1	0	1	0	0	0	1	0	0	0	
1	0	0	0	1	1	1	0	0	0	0	0	1	0	0	0	
1	0	0	1	0	0	0	0	1	0	0	0	1	0	0	0	
1	0	0	1	0	1	1	0	0	0	0	0	1	0	0	0	
1	0	0	1	1	0	1	0	0	0	0	0	1	0	0	0	
1	0	0	1	1	1	1	0	0	0	0	0	1	0	0	0	

s2	s1	s0	B1	B2	R	n0	n1	n2	L0	L1	L2	L3	L4	L5	L6	0-1 State
1	0	1	0	0	0	1	0	1	0	0	0	0	1	0	0	
1	0	1	0	0	1	1	0	0	0	0	0	0	1	0	0	
1	0	1	0	1	0	1	1	0	0	0	0	0	1	0	0	
1	0	1	0	1	1	1	0	0	0	0	0	0	1	0	0	
1	0	1	1	0	0	1	0	0	0	0	0	0	1	0	0	
1	0	1	1	0	1	1	0	0	0	0	0	0	1	0	0	
1	0	1	1	1	0	1	0	1	0	0	0	0	1	0	0	
1	0	1	1	1	1	1	0	0	0	0	0	0	1	0	0	

1	1	0	0	0	0	1	1	0	0	0	0	0	0	1	0	0-2 State
1	1	0	0	0	1	1	0	0	0	0	0	0	0	1	0	
1	1	0	0	1	0	1	1	1	0	0	0	0	0	1	0	
1	1	0	0	1	1	1	0	0	0	0	0	0	0	1	0	
1	1	0	1	0	0	1	0	1	0	0	0	0	0	1	0	
1	1	0	1	0	1	1	0	0	0	0	0	0	0	1	0	
1	1	0	1	1	0	1	1	0	0	0	0	0	0	1	0	
1	1	0	1	1	1	1	0	0	0	0	0	0	0	1	0	

1	1	1	0	0	0	1	1	1	0	0	0	0	0	0	1	0-3 State
1	1	1	0	0	1	1	0	0	0	0	0	0	0	0	1	
1	1	1	0	1	0	1	1	1	0	0	0	0	0	0	1	
1	1	1	0	1	1	1	0	0	0	0	0	0	0	0	1	
1	1	1	1	0	0	1	1	1	0	0	0	0	0	0	1	
1	1	1	1	0	1	1	0	0	0	0	0	0	0	0	1	
1	1	1	1	1	0	1	1	1	0	0	0	0	0	0	1	
1	1	1	1	1	1	1	0	0	0	0	0	0	0	0	1	

Boolean Expressions:

$$L0 = s2's1's0$$

$$L1 = s2's1's0'$$

$$L2 = s2's1's0$$

$$L3 = s2's1's0'$$

$$L4 = s2s1's0$$

$$L5 = s2s1's0'$$



$$L6 = s2s1's0$$


$$n2 = B1'R + B2'R + S0R + S1R + s2B1' + s2B2 + s2s1 + s1's0 B1'B2 + s2s0 \\ R(B1' + B2' + s0 + s1) + s2(B1' + B2 + s1's0) s1's0 B1'B2$$

$$n1 = s1s0R' + s2's1 B2 R' + s1 B1 B2 R' + s2s1 B1'R' + s2's0 B1 B2'R' + s2s0 B1'B2 R'$$


$$n0 = s0 B1' B2'R' + s0 B1 B2 R' + s1 B1' B2 R' + s1 B1 B2'R' + s2s0'B1' B2 R' + s2s0'B1 B2'R'$$

Combinational Logic

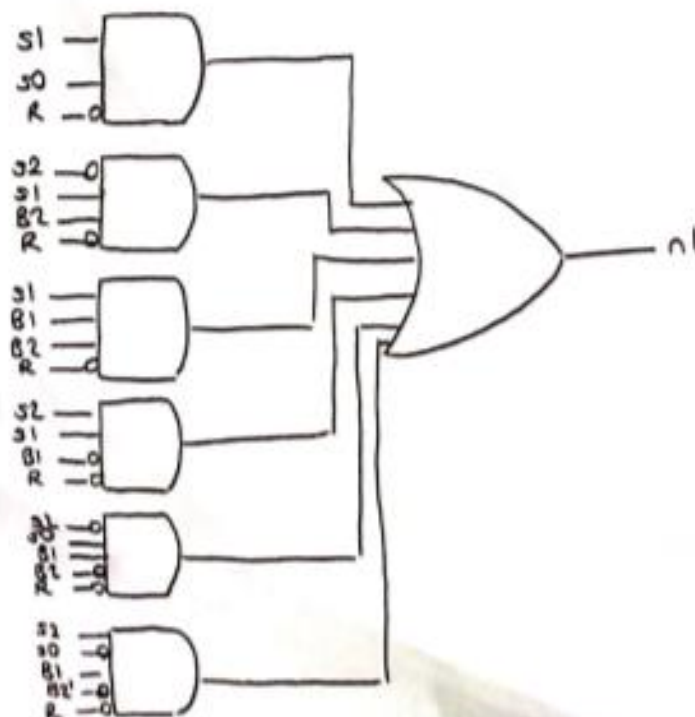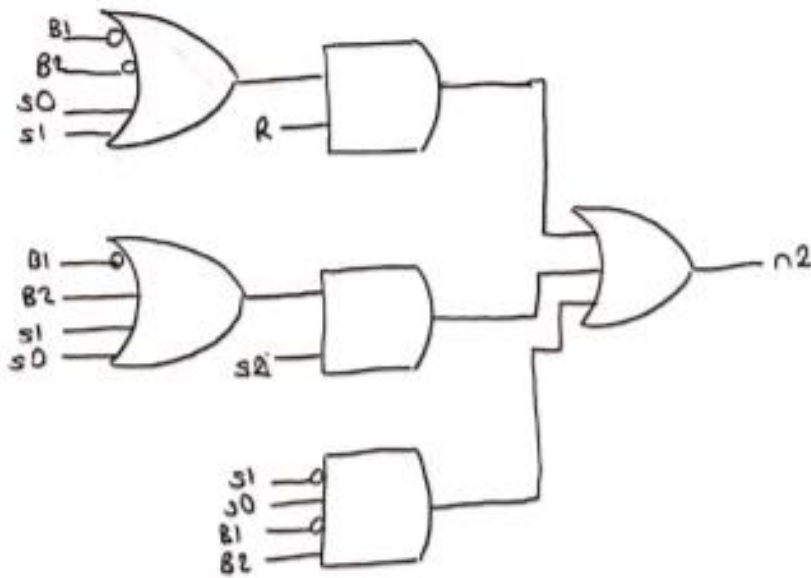

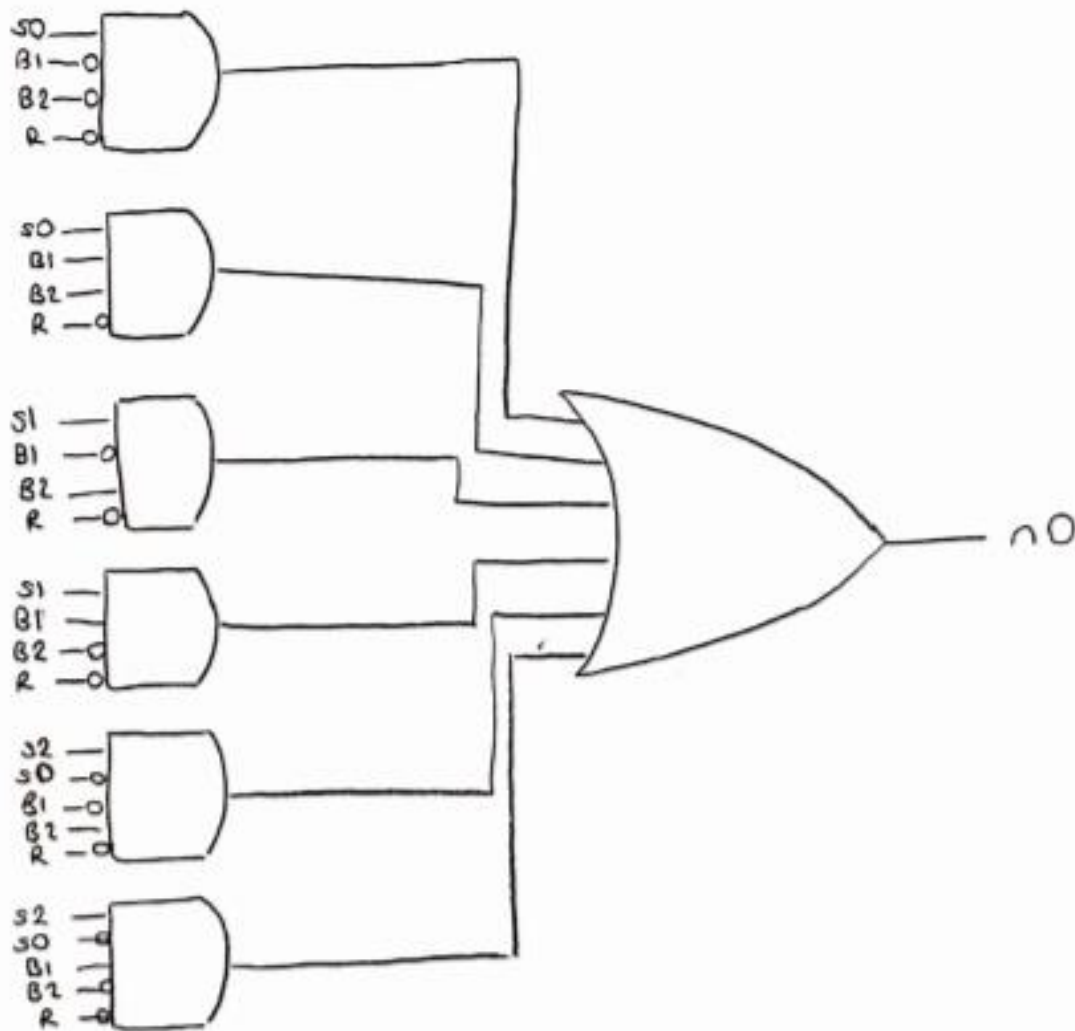


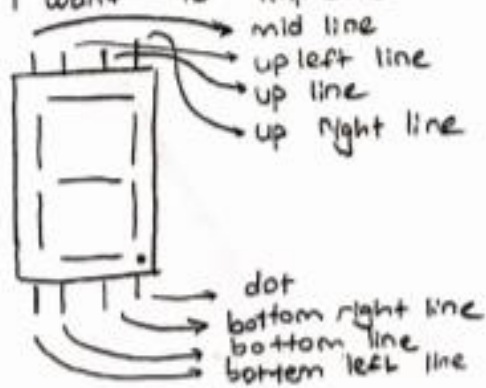I want to implement a FSM that uses 7-segment display




There will be two inputs and 7 outputs
and state register will be 3-bit


Start State: No leds are not open

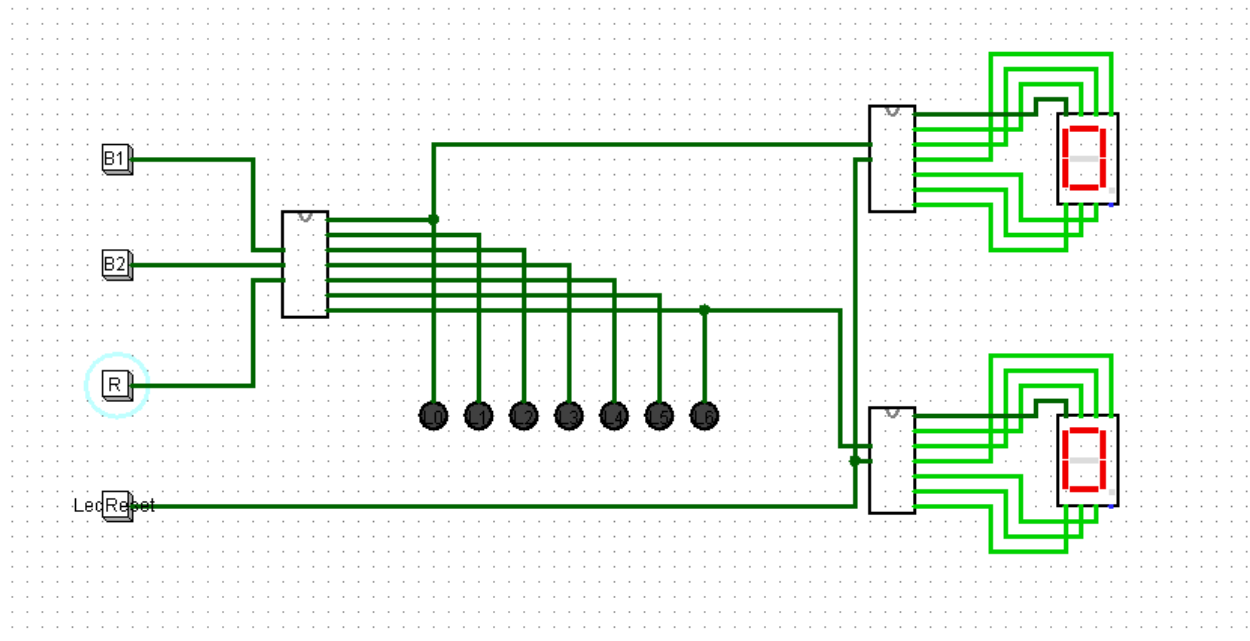


Press Reset: Game Start

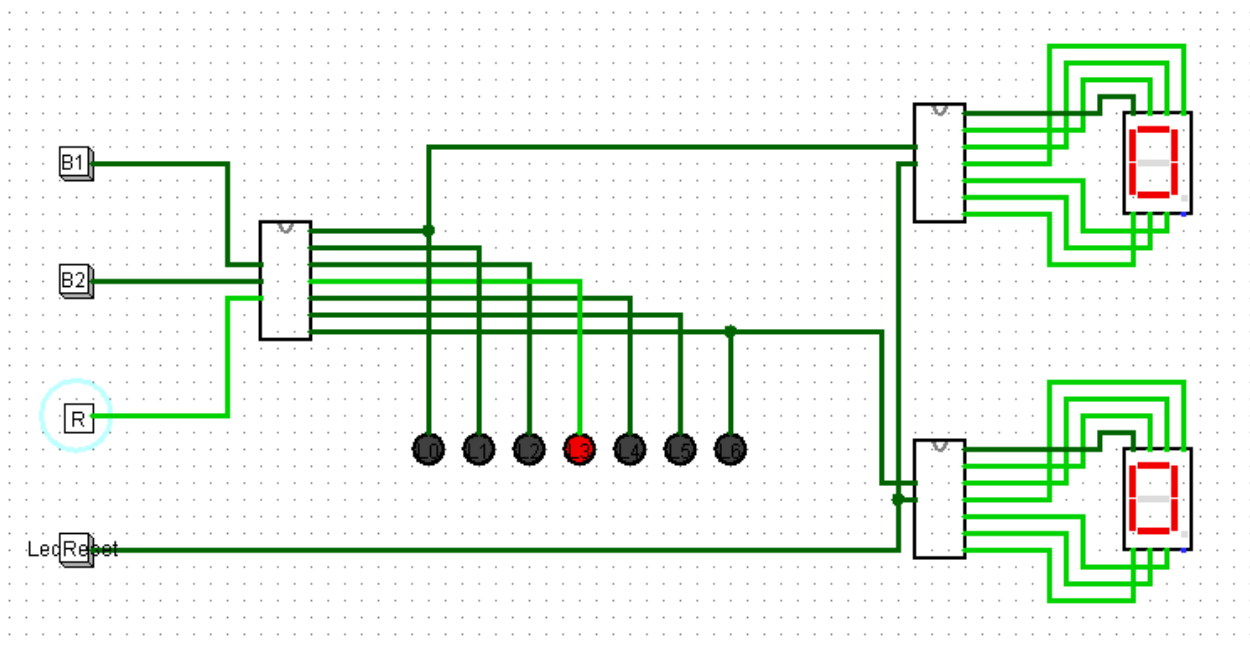


Press B1: Goes the left side

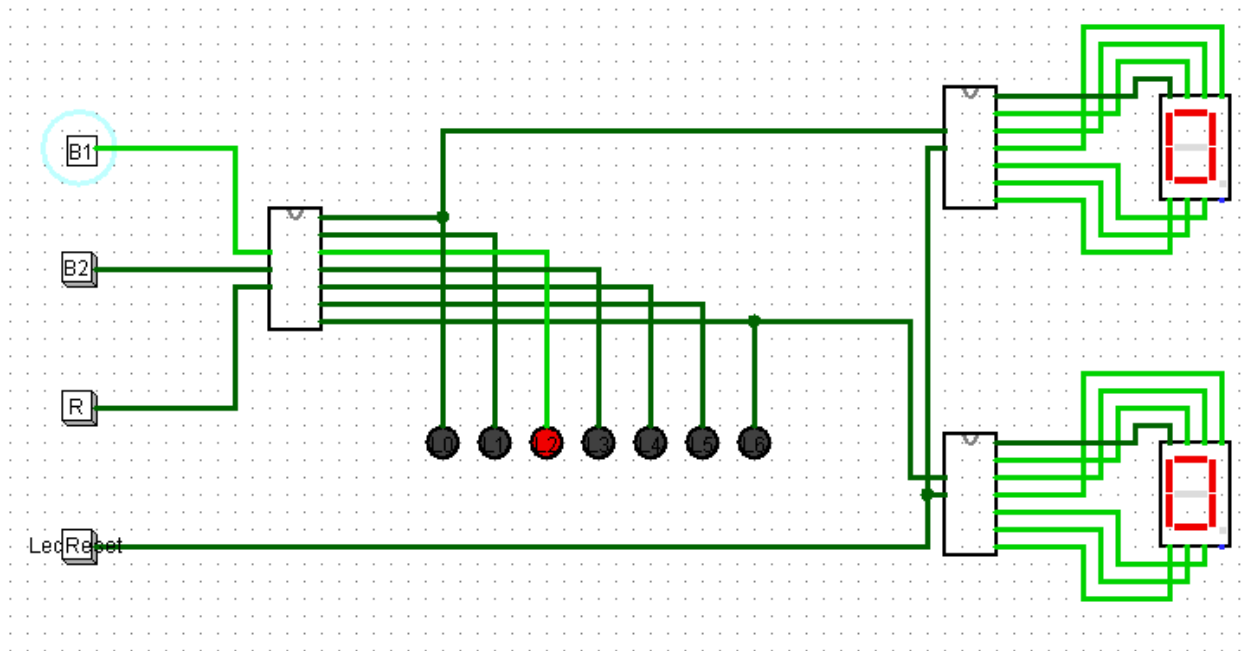


Press B1 and B2: Nothing changed

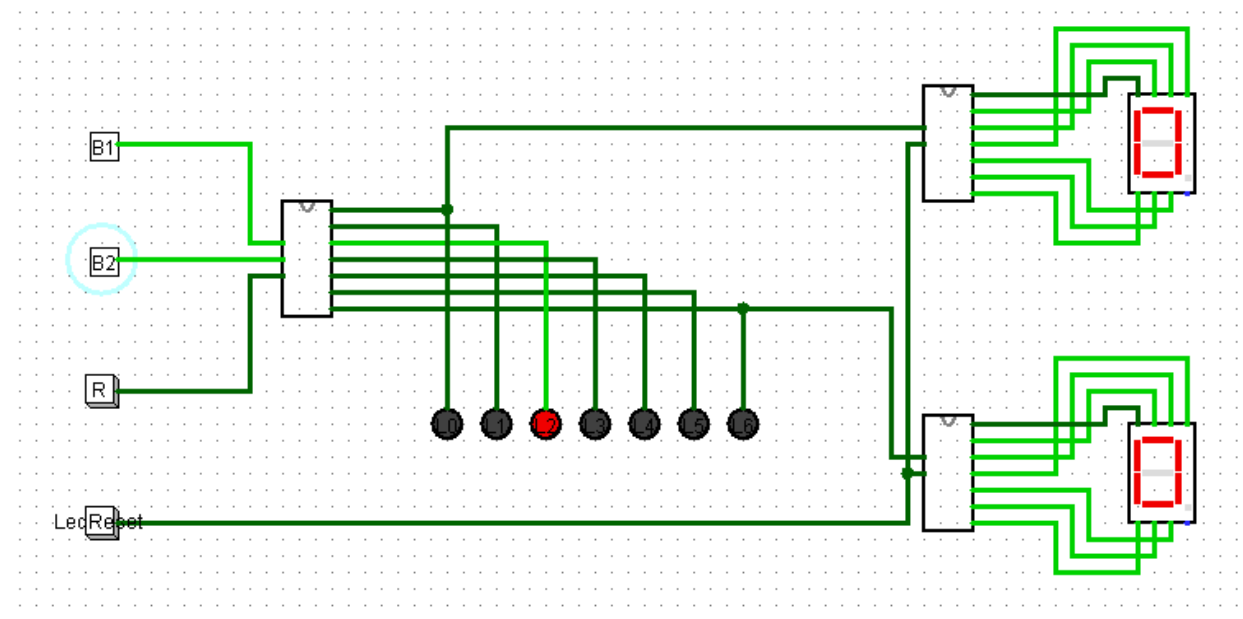


Press B1: Goes left

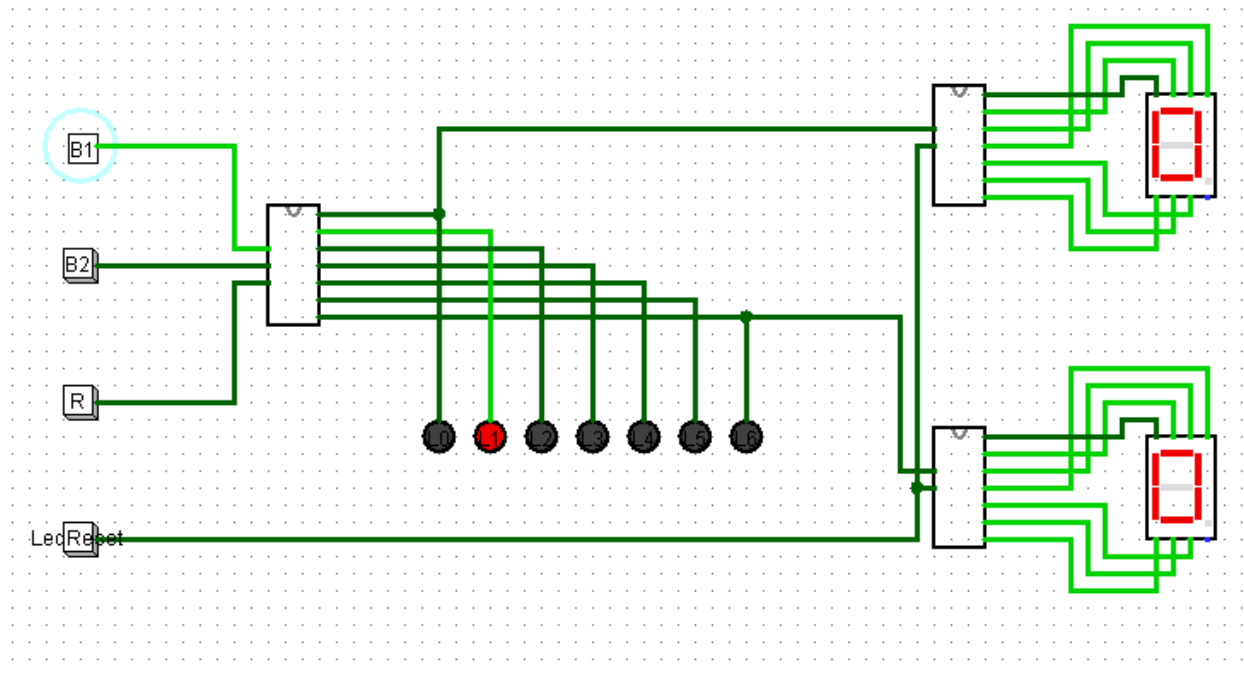

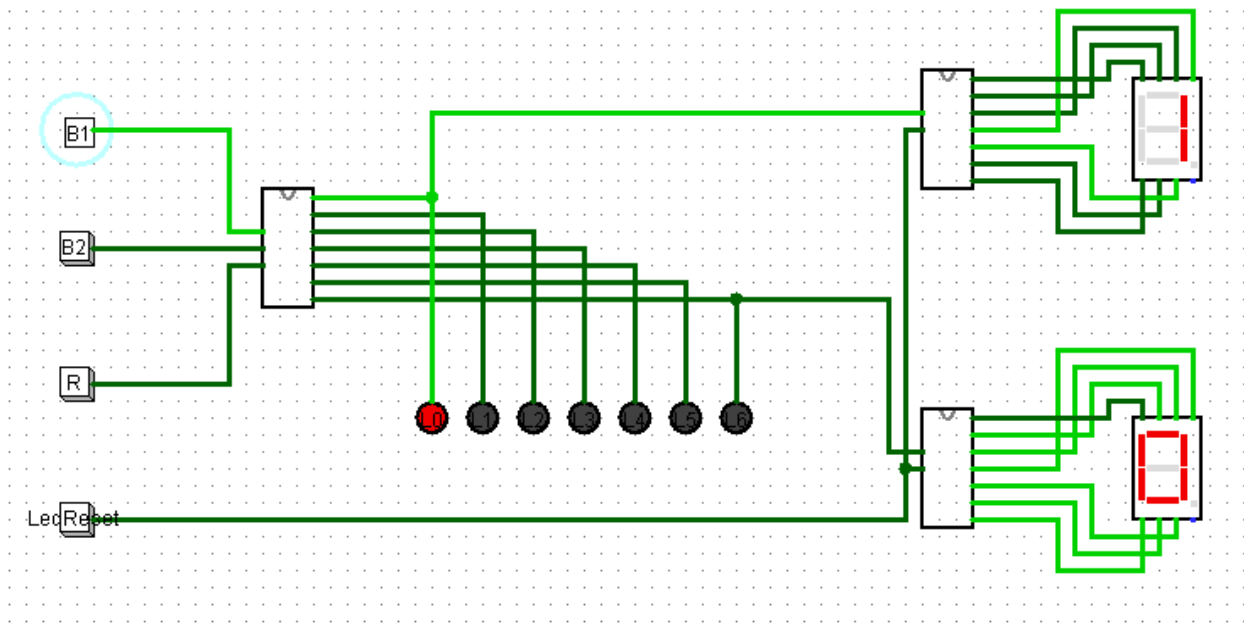
Press B1: Goes L0 and first led displays 1



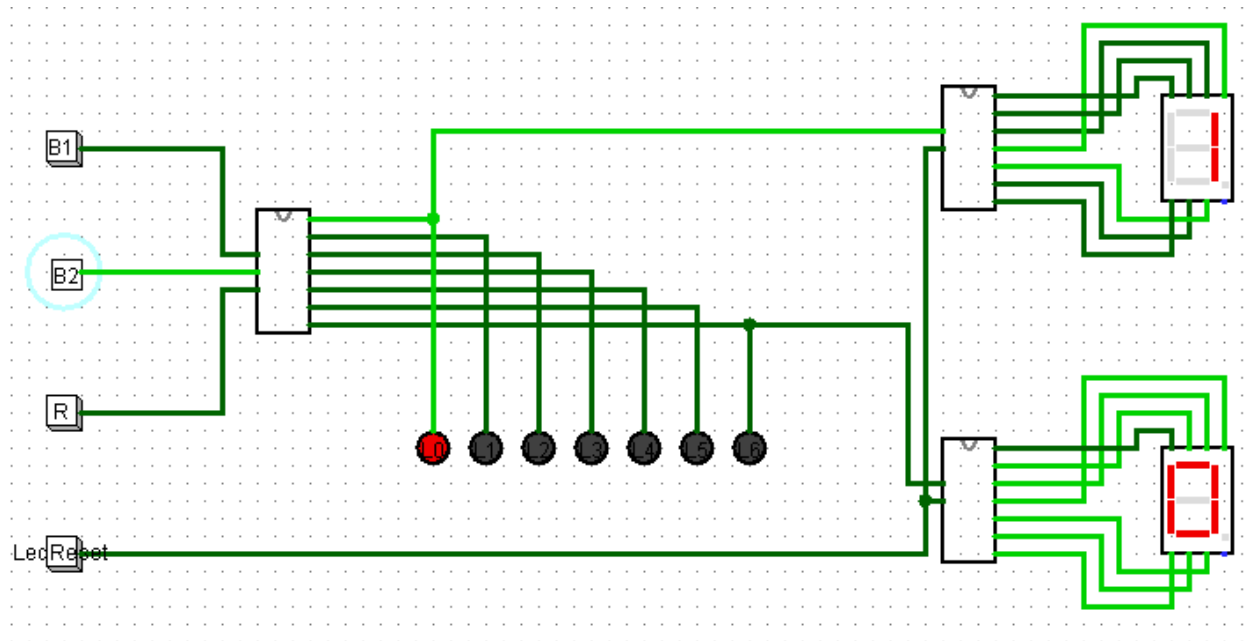
Press B2: Nothing changes because player 1 won.




Press R: Resets light

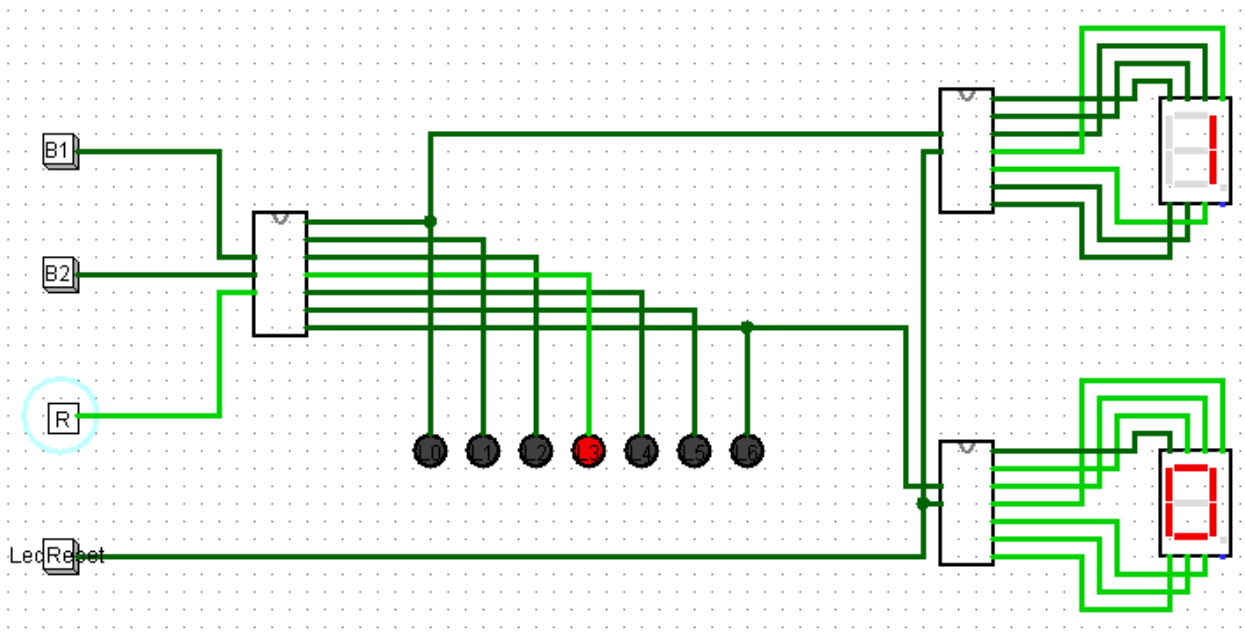

Press B1, B2 and R: Resets light

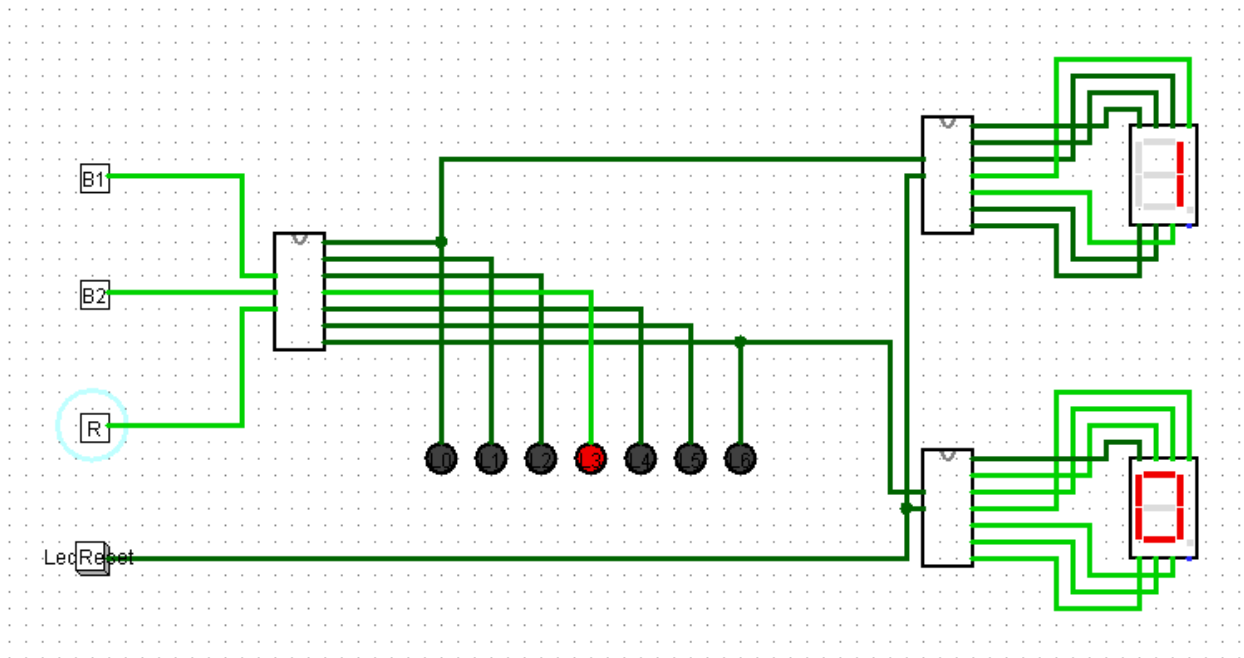


Press Led_Reset: Both leds display 0

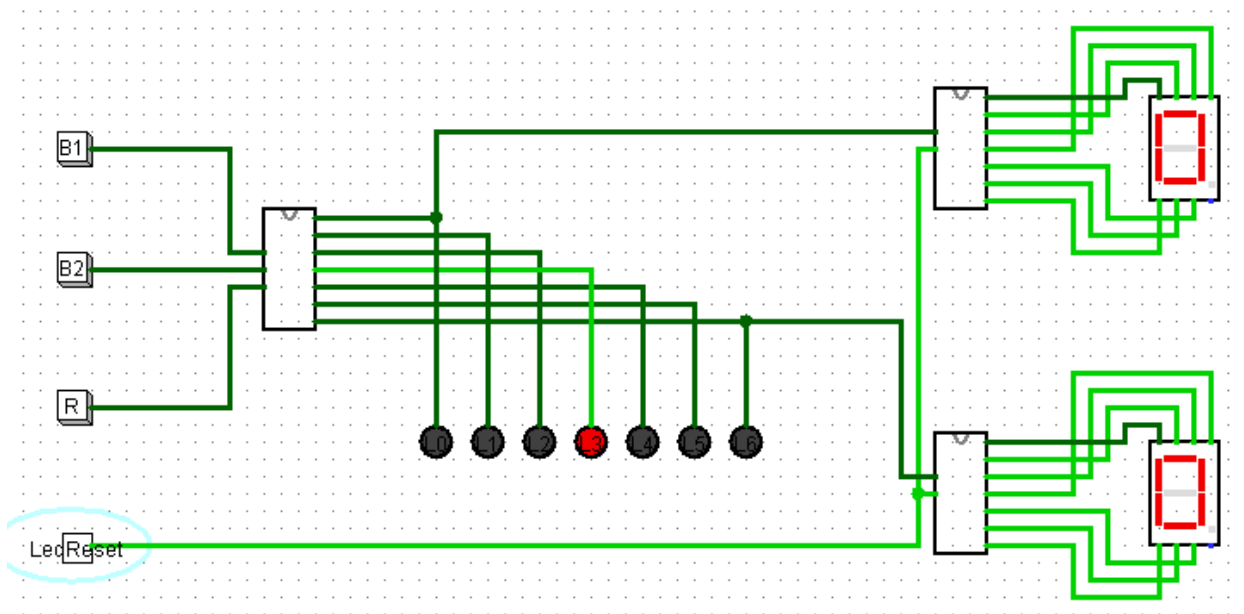

Inputs: R, X, s3, s2, s1, s0

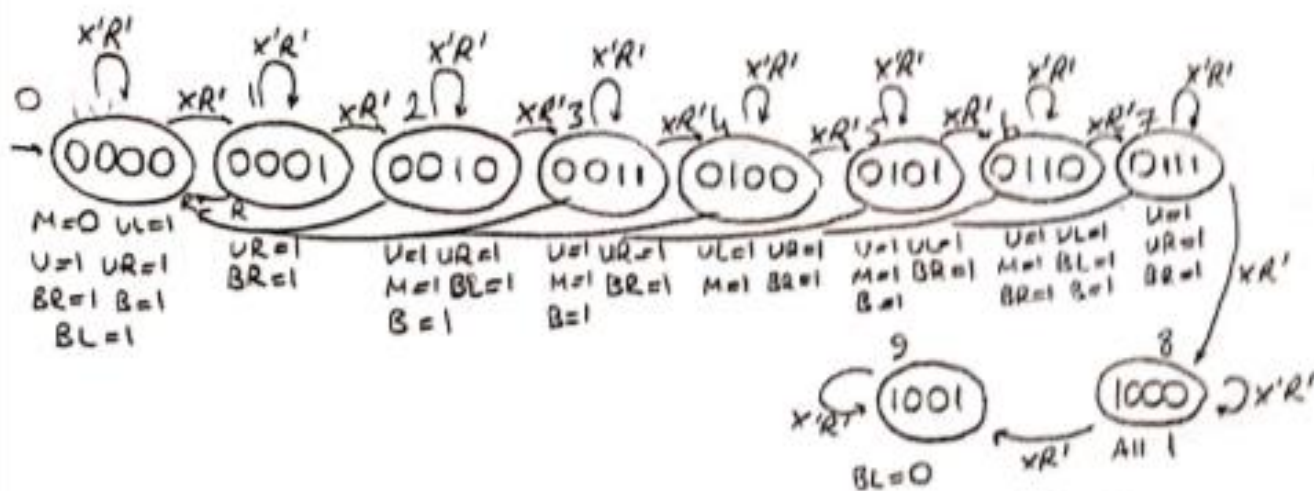Outputs: n3, n2, n1, n0, M, UL, U, UR, BR, B, BL



s3	s2	s1	s0	R	X	n3	n2	n1	n0	M	UL	U	UR	BR	B	BL
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
0	0	0	0	0	1	0	0	0	1	0	1	1	1	1	1	1
0	0	0	0	1	0	0	0	0	0	1	1	1	1	1	1	1
0	0	0	0	1	1	0	0	0	0	1	1	1	1	1	1	1
0	0	0	1	0	0	0	0	1	0	1	1	1	1	1	0	0
0	0	0	1	0	1	0	0	1	0	0	0	1	1	1	0	0
0	0	0	1	1	0	0	0	0	0	1	1	1	1	1	1	1
0	0	0	1	1	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	0	0	0	1	0	1	1	1	1	1	1	1
0	0	1	0	0	1	0	0	1	0	0	1	1	1	1	1	1
0	0	1	0	1	0	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	1	1	0	0	0	0	1	1	1	1	1	1	1
0	1	0	0	0	0	0	1	0	0	1	1	0	1	1	0	0
0	1	0	0	0	1	0	1	0	0	1	1	1	1	1	1	1
0	1	0	0	1	0	0	0	0	0	1	1	1	1	1	1	1
0	1	0	0	1	1	0	0	0	0	1	1	1	1	1	1	1

0 □

1 □

2 □

3 □

4 □

s3	s2	s1	s0	R	x	n3	n2	n1	n0	M	UL	U	UR	BR	B	BL	
0	1	0	1	0	0	0	1	0	1	1	1	1	1	1	1	1	1
0	1	0	1	0	1	0	1	1	0	1	1	1	0	1	1	0	1
0	1	0	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	1	1	1	0	0	0	0	1	1	1	1	1	1	1	1
0	1	1	0	0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	1	1	0	0	1	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	0	1	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	1	0	1	1	0	0	0	0	1	1	1	1	1	1	1	1
0	1	1	1	0	0	0	1	1	1	1	1	1	1	1	1	1	1
0	1	1	1	0	1	1	0	0	0	0	0	1	1	1	0	0	1
0	1	1	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	1	1	1	1	1	1	1	1
0	0	0	0	0	0	1	0	0	0	1	1	1	1	1	1	1	1
0	0	0	0	0	1	1	0	1	0	1	1	1	1	1	1	1	1
0	0	0	0	1	0	0	0	0	0	1	1	1	1	1	1	1	1
0	0	0	0	1	1	0	0	0	0	1	1	1	1	1	1	1	1
0	0	0	1	0	0	1	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	0	1	1	0	0	1	1	1	1	1	1	1	0	1
0	0	0	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1
0	0	0	1	1	1	0	0	0	0	1	1	1	1	1	1	1	1

I did not convert this to boolean expressions. In Logisim program, it's automatically converts truth table to logic gates.