

Project 2

171044032



Türker Tercan

C code :

```


1- while (!calculate);
2- a = a-in;
3- b = b-in;
4- mult = 0;
5- while (a > 0) {
6-   mult = mult + b;
7-   a = a - 1;
8- }

```

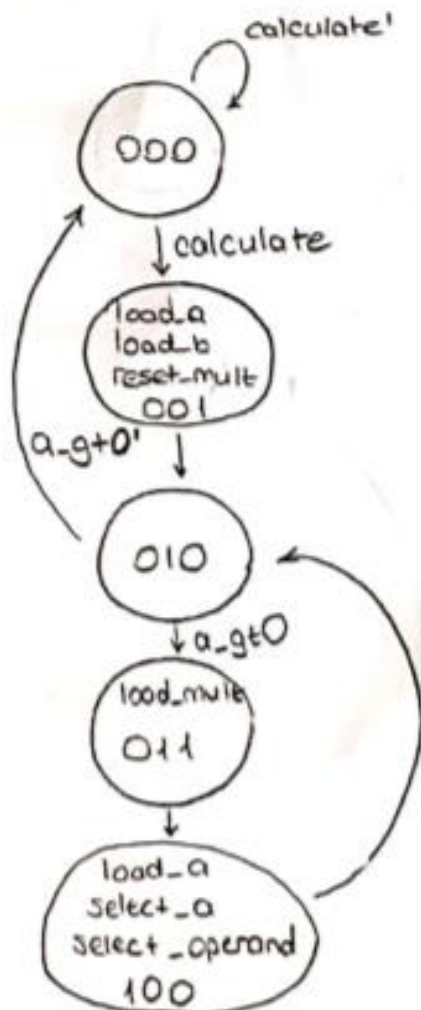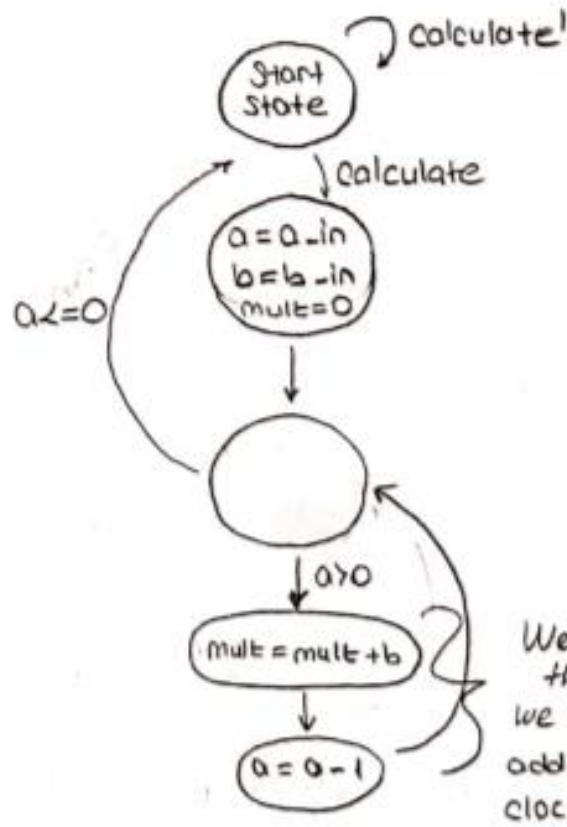State Diagram :Early FSMsDatapath :

- We need 3 registers for a, b and mult.
- We can only use one adder unit
- Use three muxes, one for loading a, rest of them will be used for adder
- And one comparator for is a greater than 0

Draw Datapath:

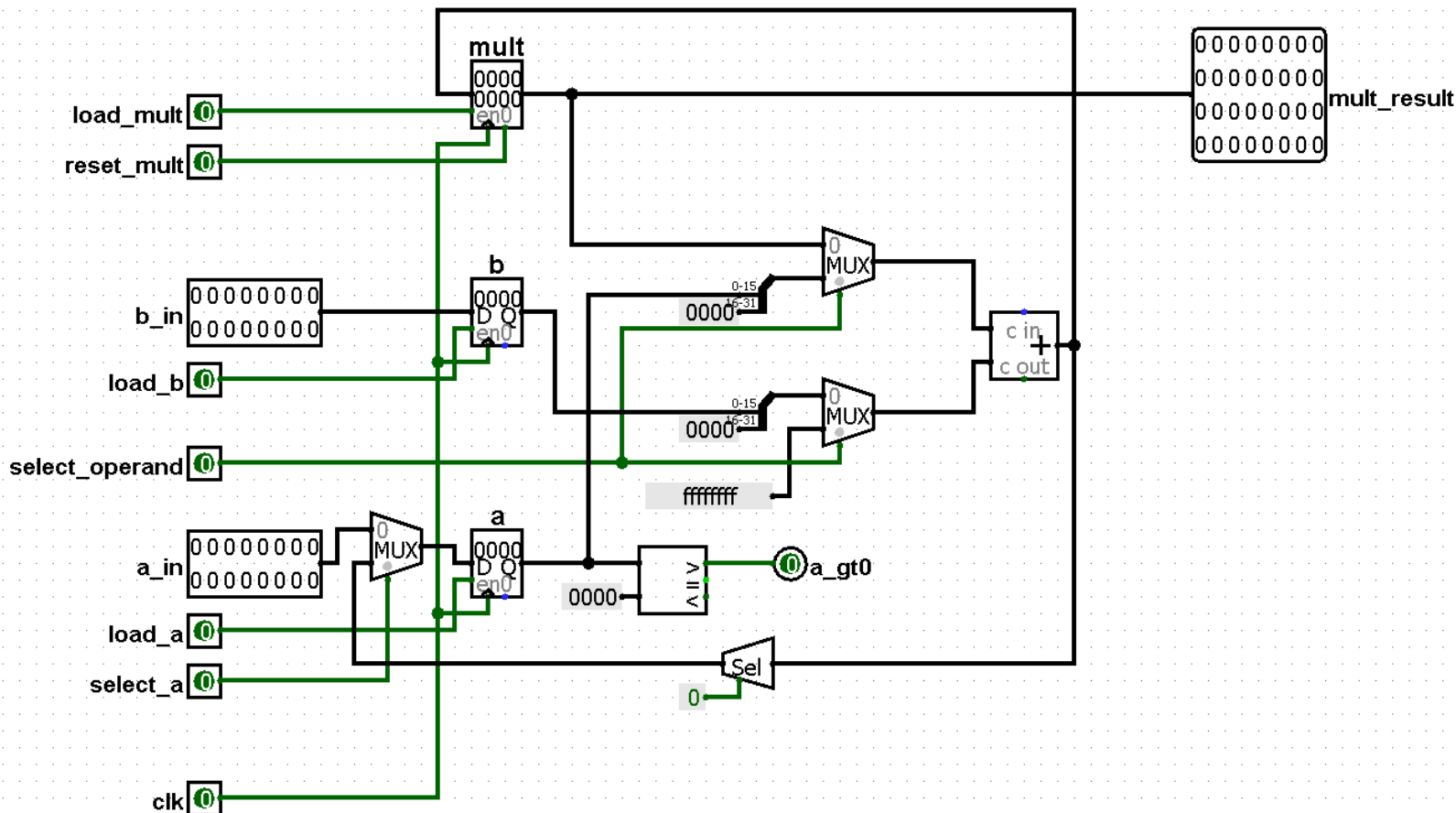

Boolean Expression :

Present State			Inputs		Next State		
P2	P1	P0	a-gt0	calculate	N2	N1	N0
0	0	0	—	0	0	0	0
0	0	0	—	1	0	0	1
0	0	1	—	—	0	1	0
0	1	0	0	—	0	0	0
0	1	0	1	—	0	1	1
0	1	1	—	—	1	0	0
1	0	0	—	—	0	1	0

$$N2 = P2' P1 P0$$

$$N1 = P2' P1' P0 + P2' P1 P0' a_gt0 + P2 P1' P0'$$

$$N0 = P2' P1' P0' calculate + P2' P1 P0' a_gt0$$

$$= P2' P0' (P1' calculate + P1 a_gt0)$$


$$N1 = P2' P1' P0 + P2' P1 P0' a_gt0 + P2 P1' P0'$$

Present State				Outputs					
	P2	P1	P0	load_a	load_b	reset_mult	load_mult	select_a	select_operand
s0	0	0	0	0	0	0	0	0	0
s1	0	0	1	1	1	1	0	0	0
s2	0	1	0	0	0	0	0	0	0
s3	0	1	1	0	0	0	1	0	0
s4	1	0	0	1	0	0	0	1	1


$$\begin{aligned} \text{load_a} &= s1 + s4 & \text{reset_mult} &= s1 & \text{select_a} &= s4 \\ \text{load_b} &= s1 & \text{load_mult} &= s3 & \text{select_operand} &= s4 \end{aligned}$$

* After i designed datapath, i realized there is no need to use reset_mult and select_operand because load_b = reset_mult and select_a = select_operand, so i decided to not to use them.


Optimized Datapath:

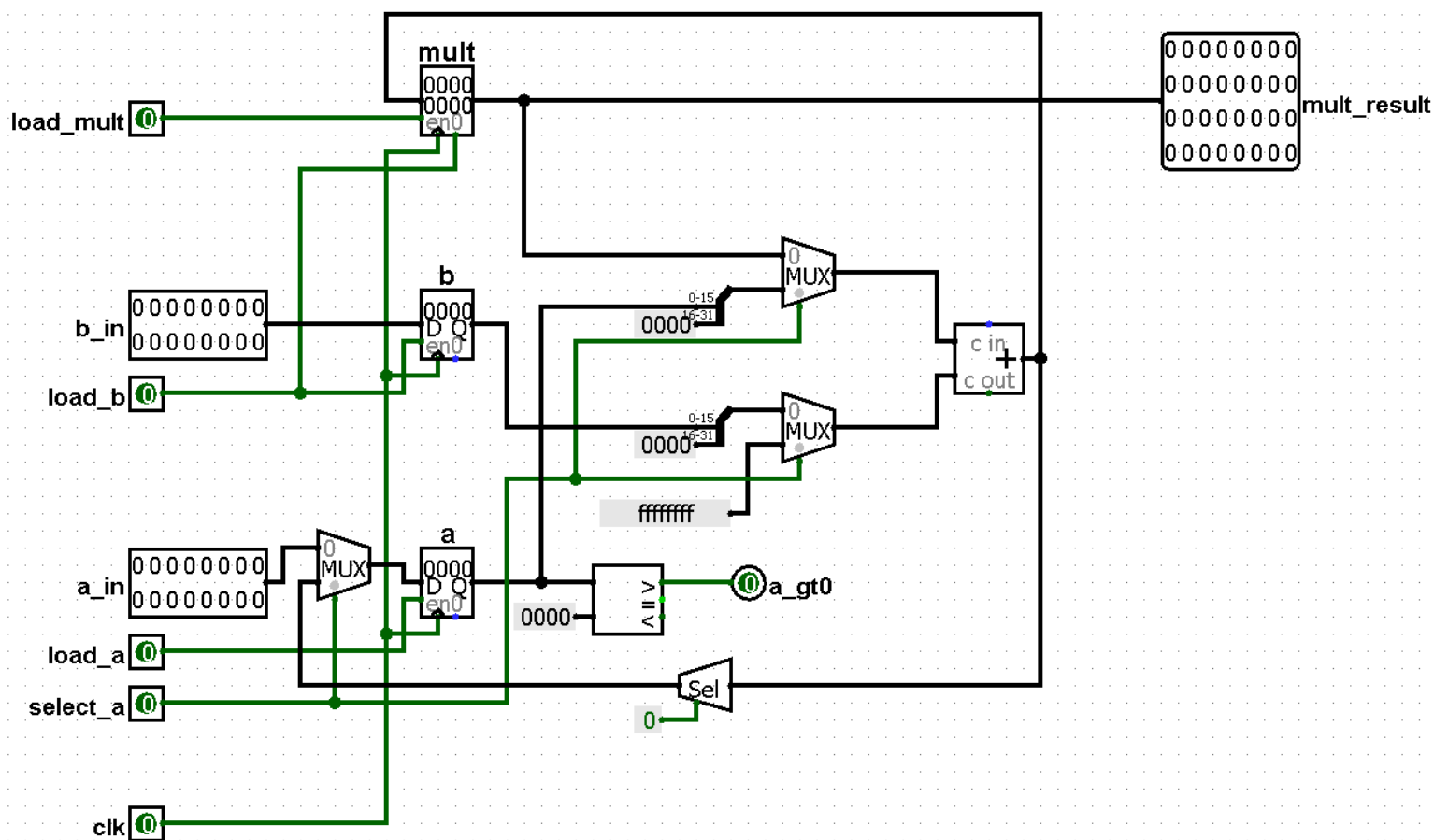


Control Unit:

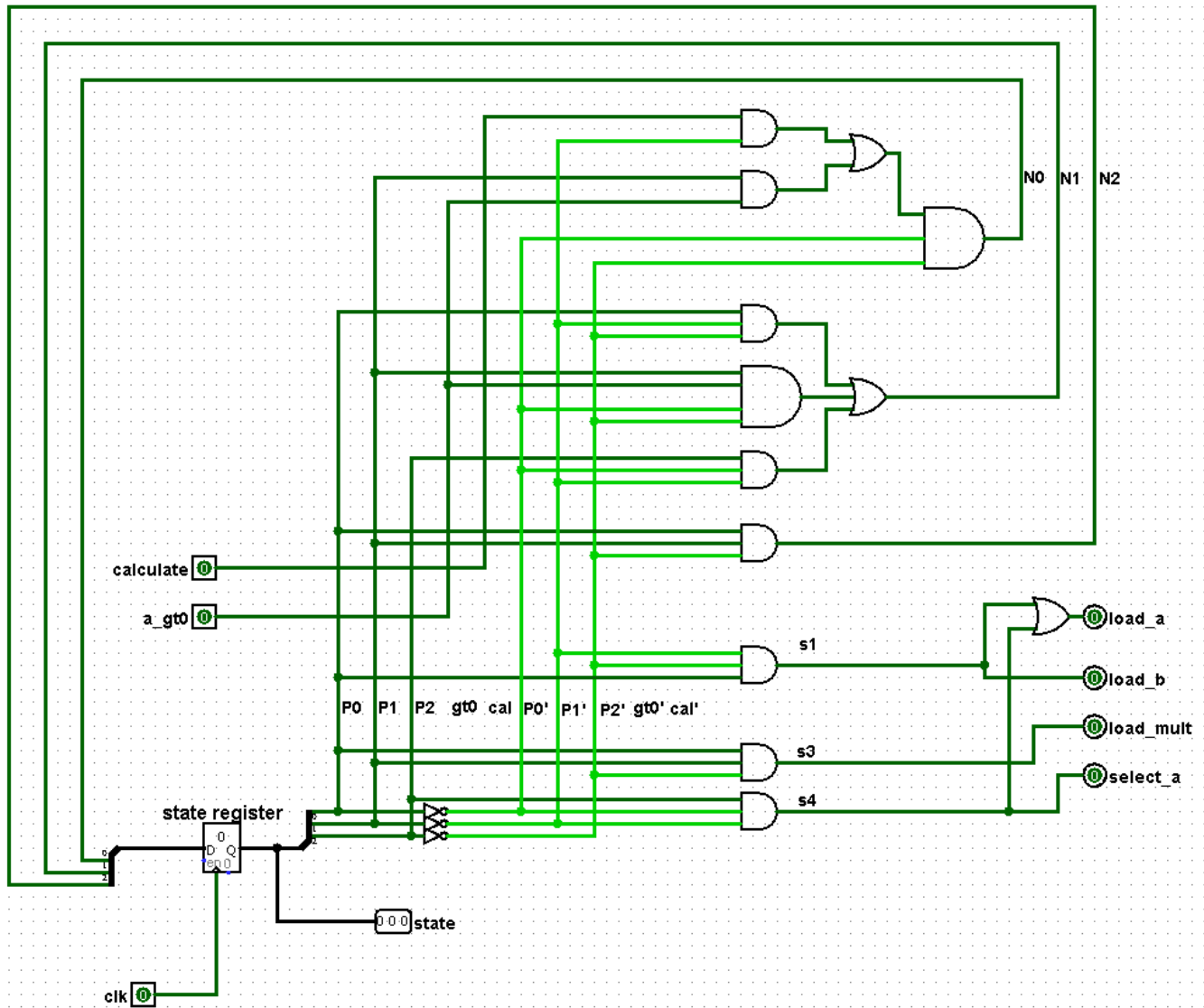

FSM:

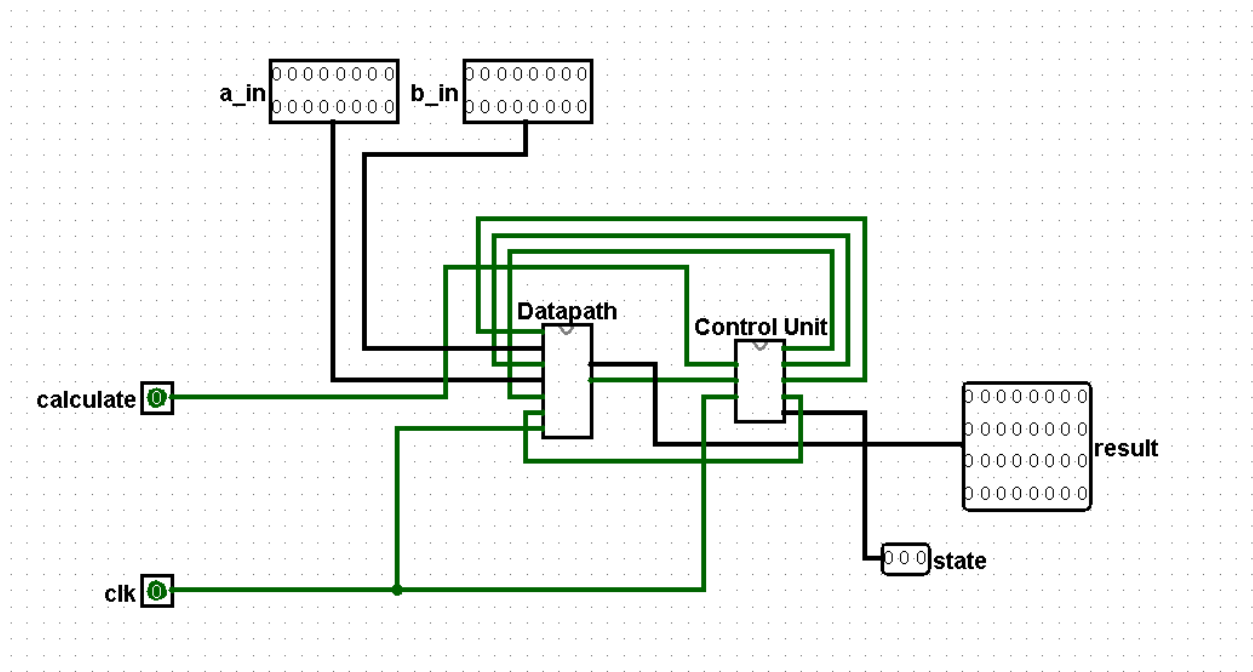

Main:

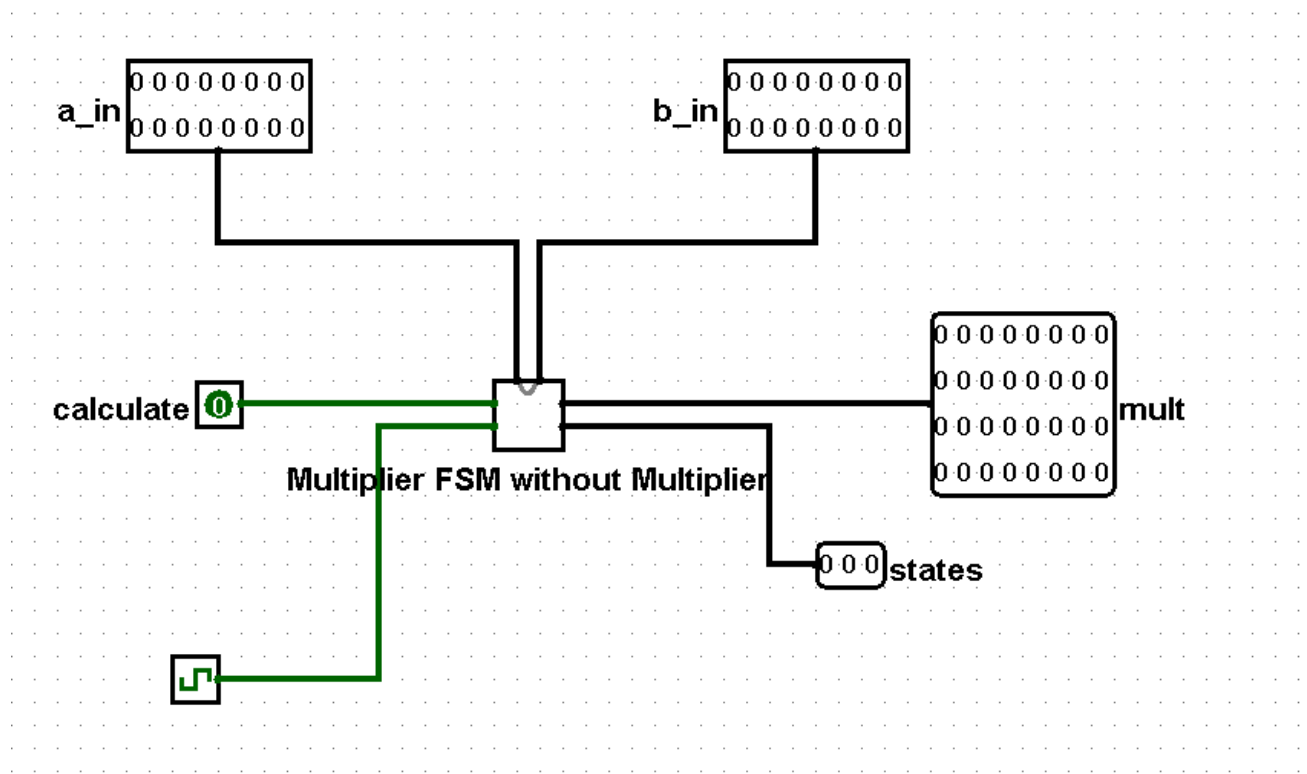

Simulation:

- This FSM does not work non positive integers.


Test Case: Work on positive integers

Test Data: a_in = 7, b_in = 43, mult = ?


Excepted Result: mult = 301

Simulation:


- Set up the inputs

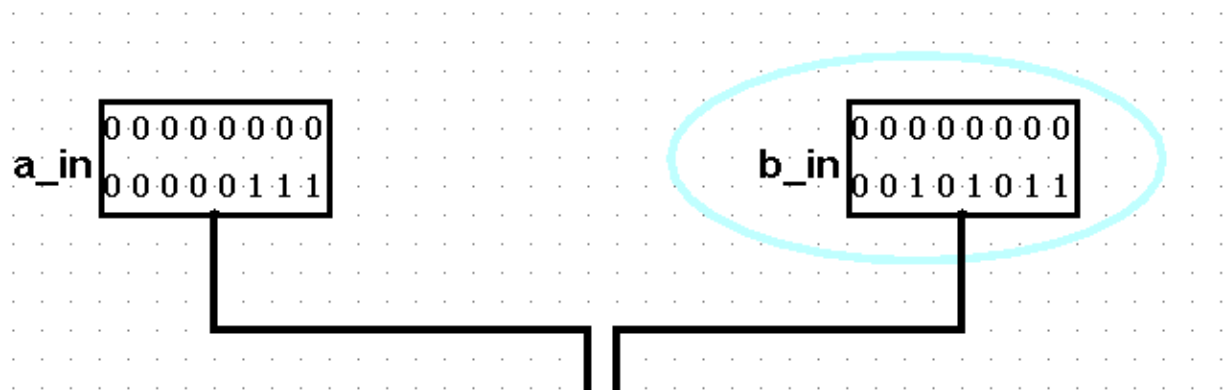

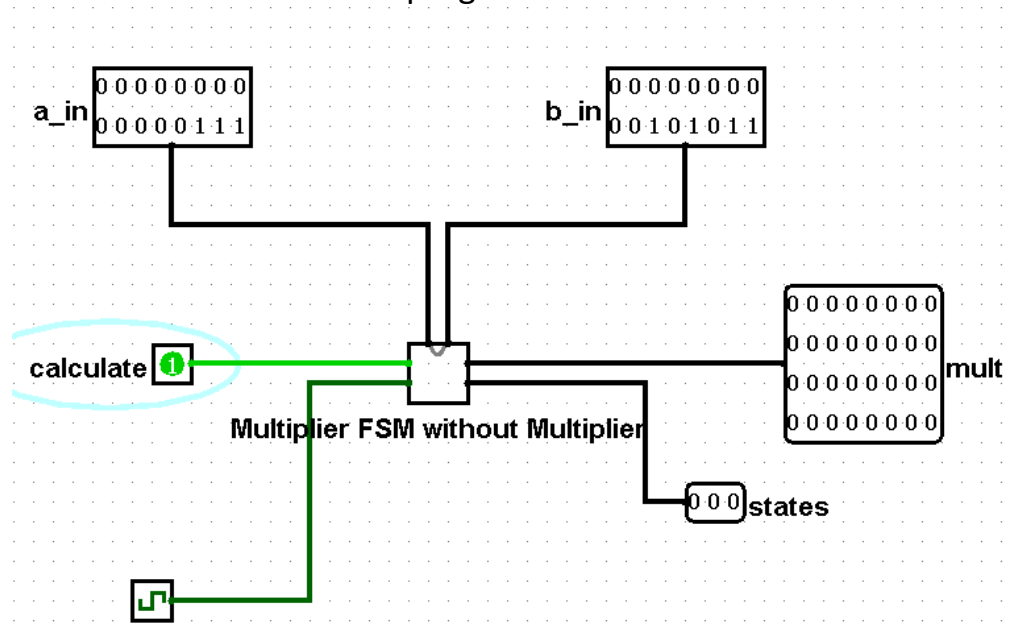
- Press calculate and program will do the rest




- Enters first state

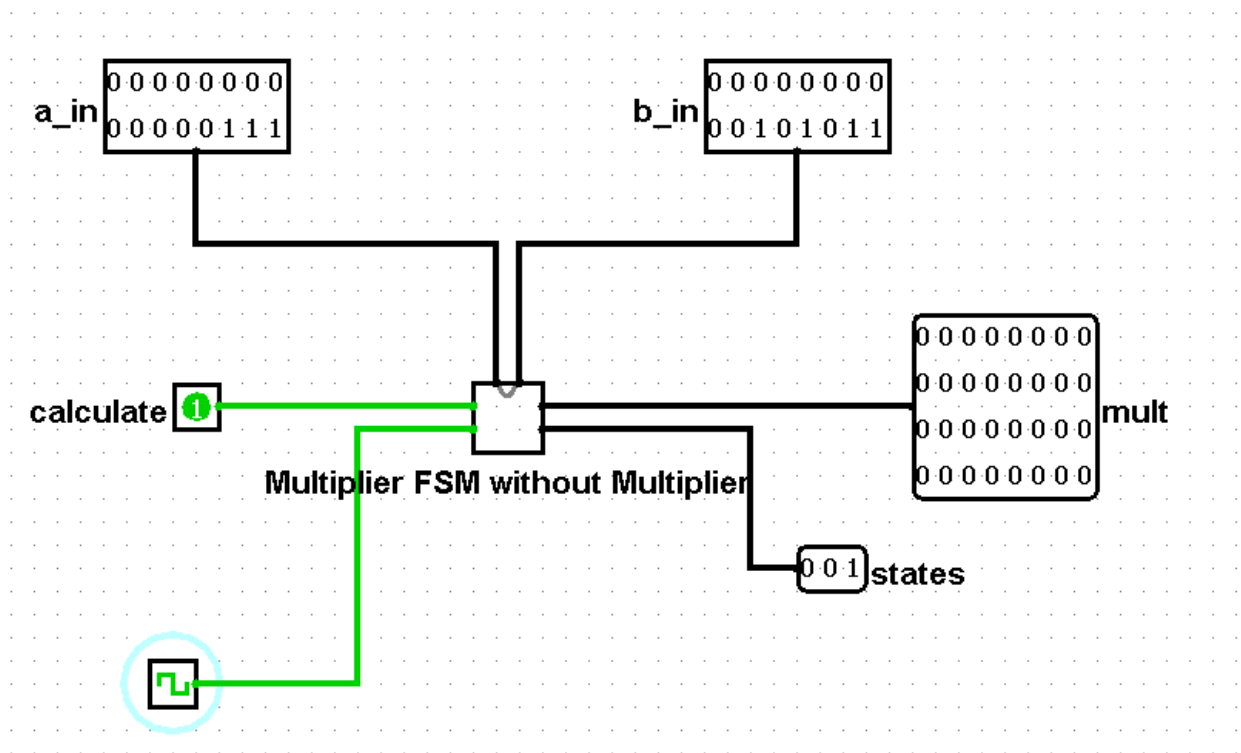


- Second state

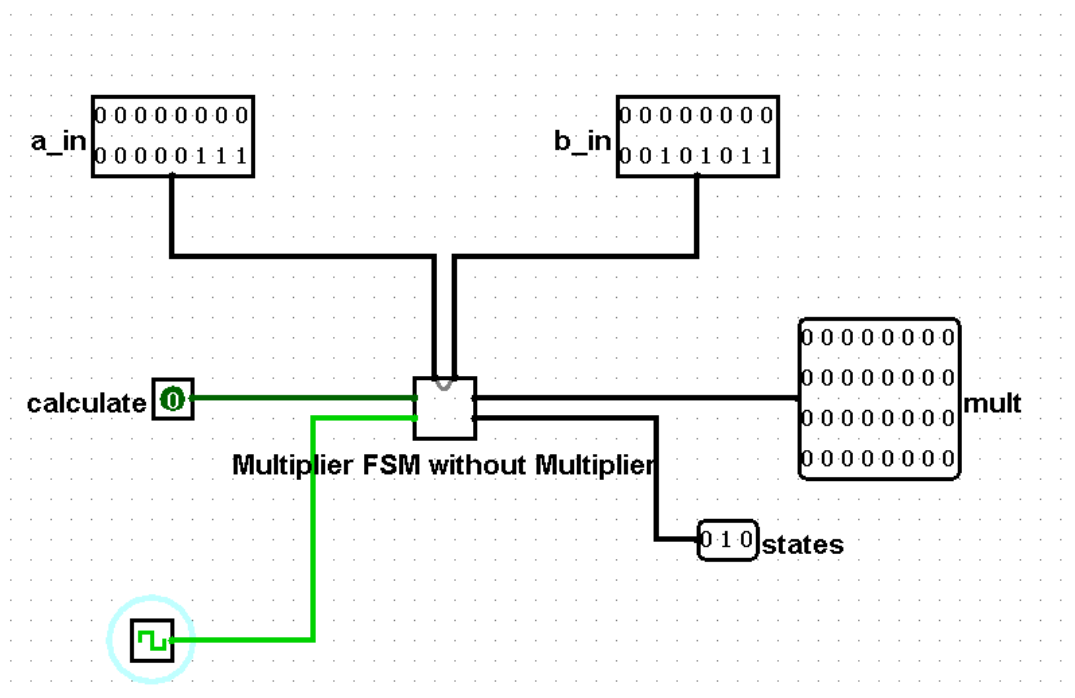


- Third state


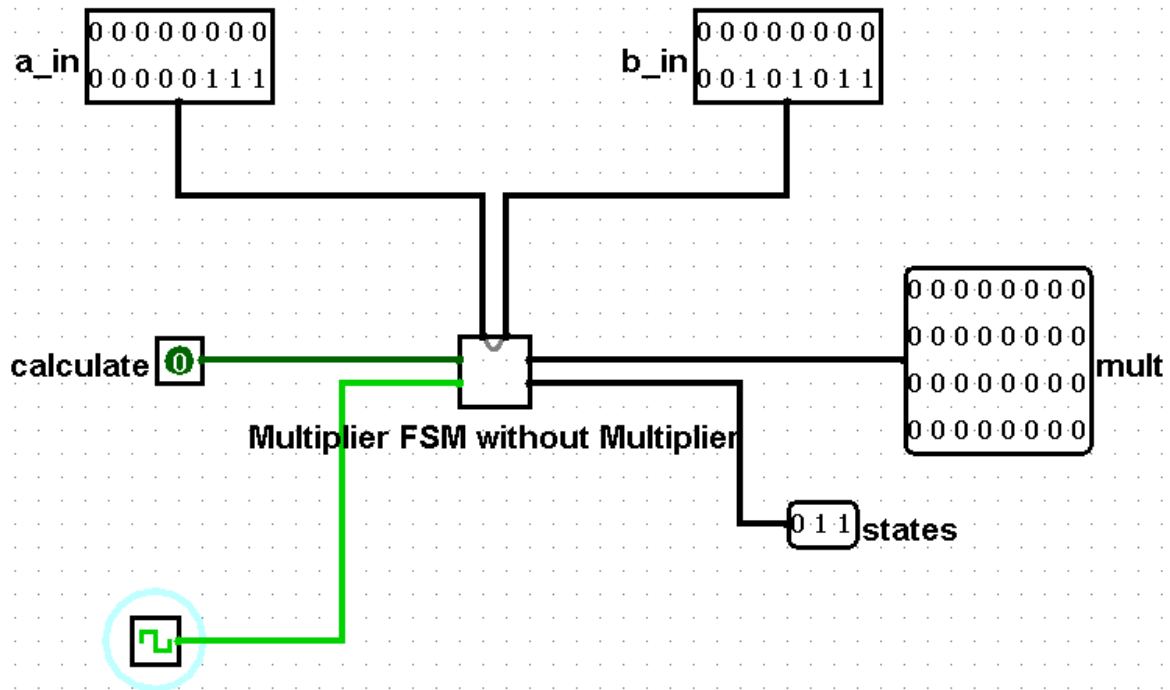


- Fourth state

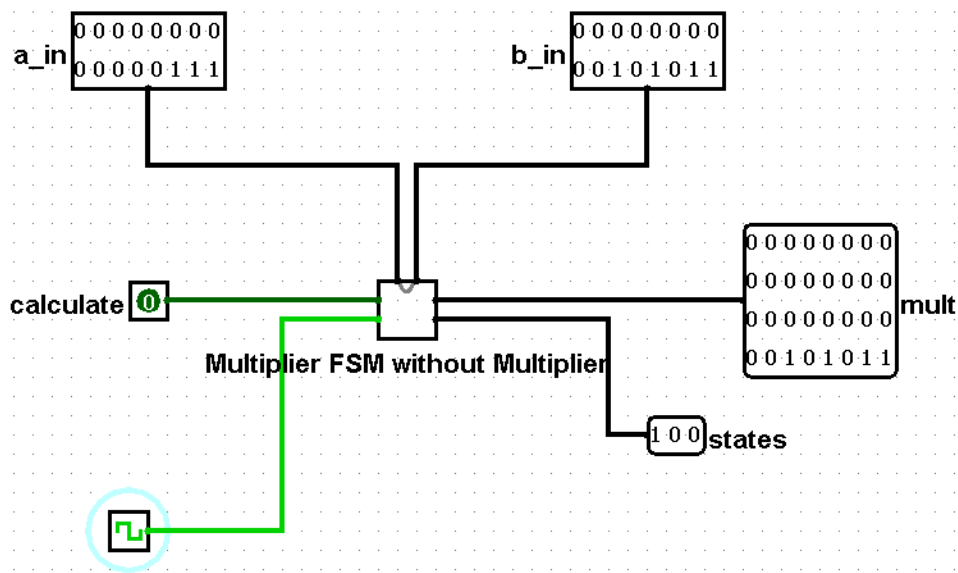


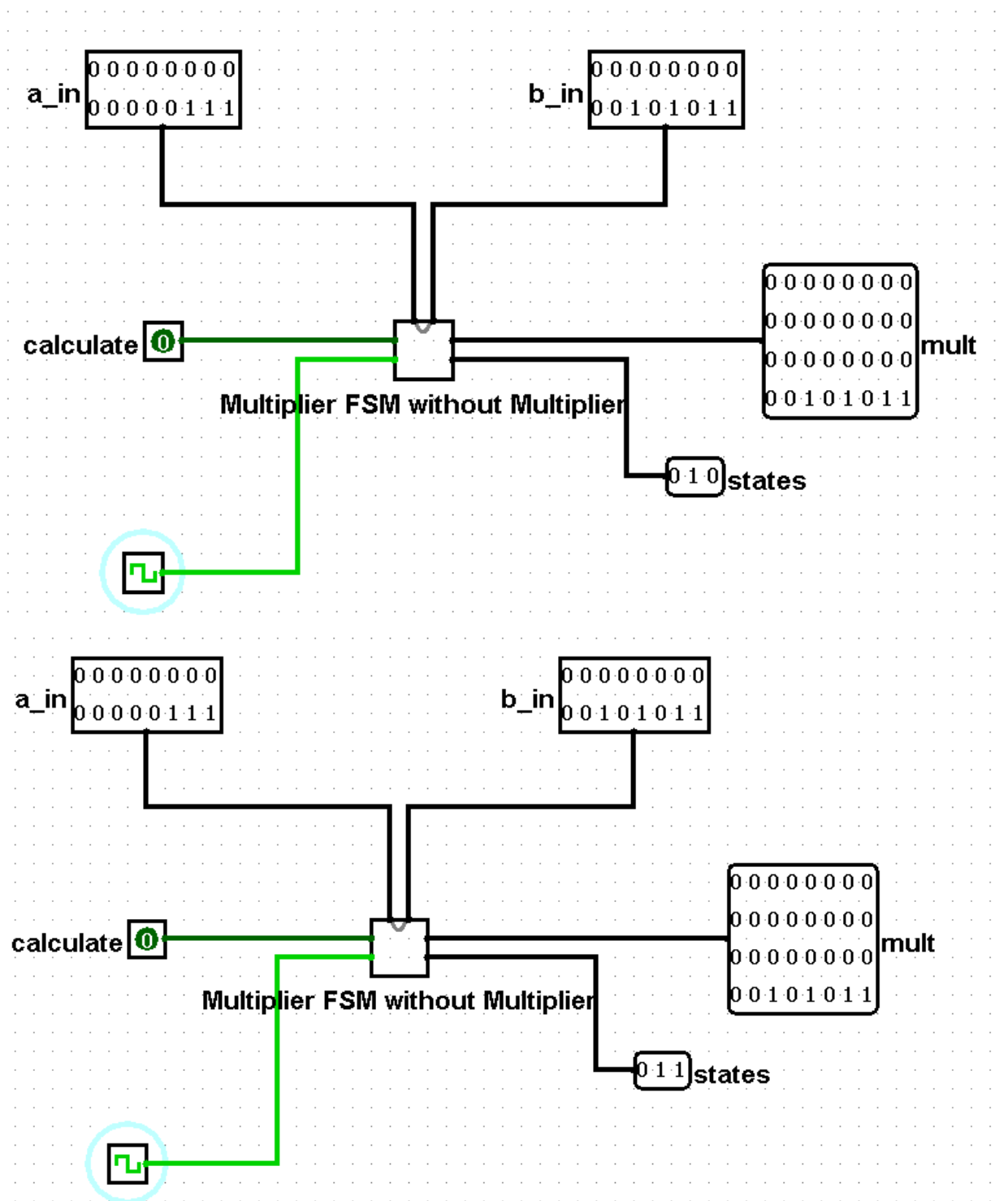- As you can see, addition added to mult and after this state, it should return to state 2 and it will continue to loop until a_register equals to zero.



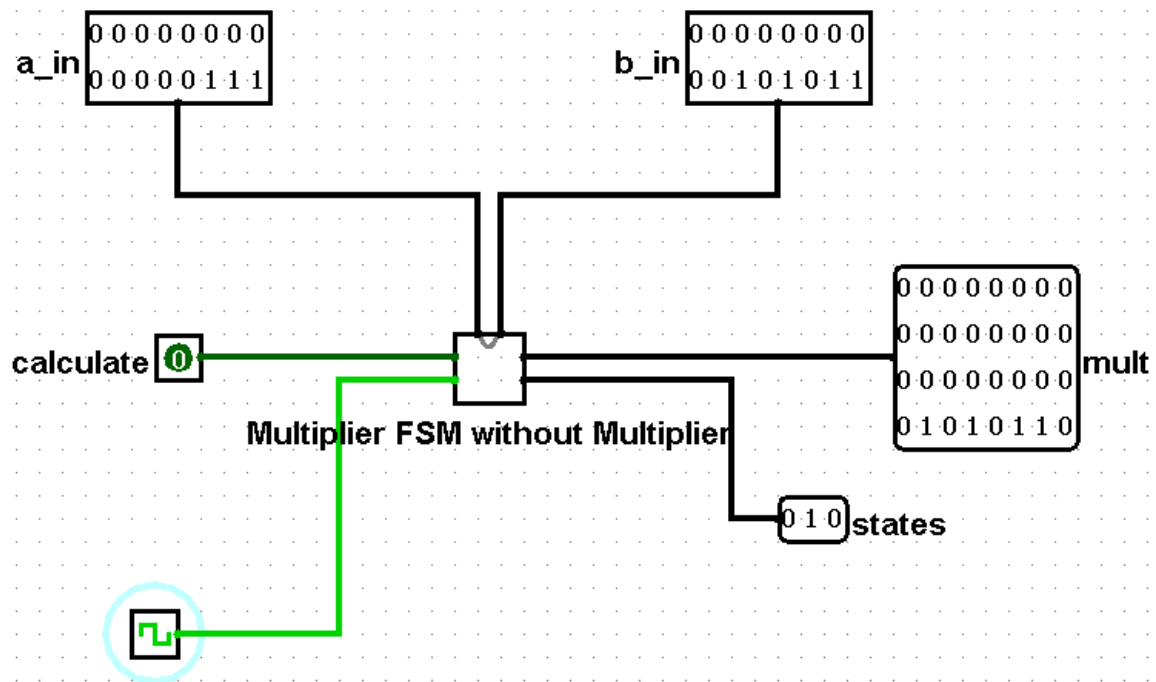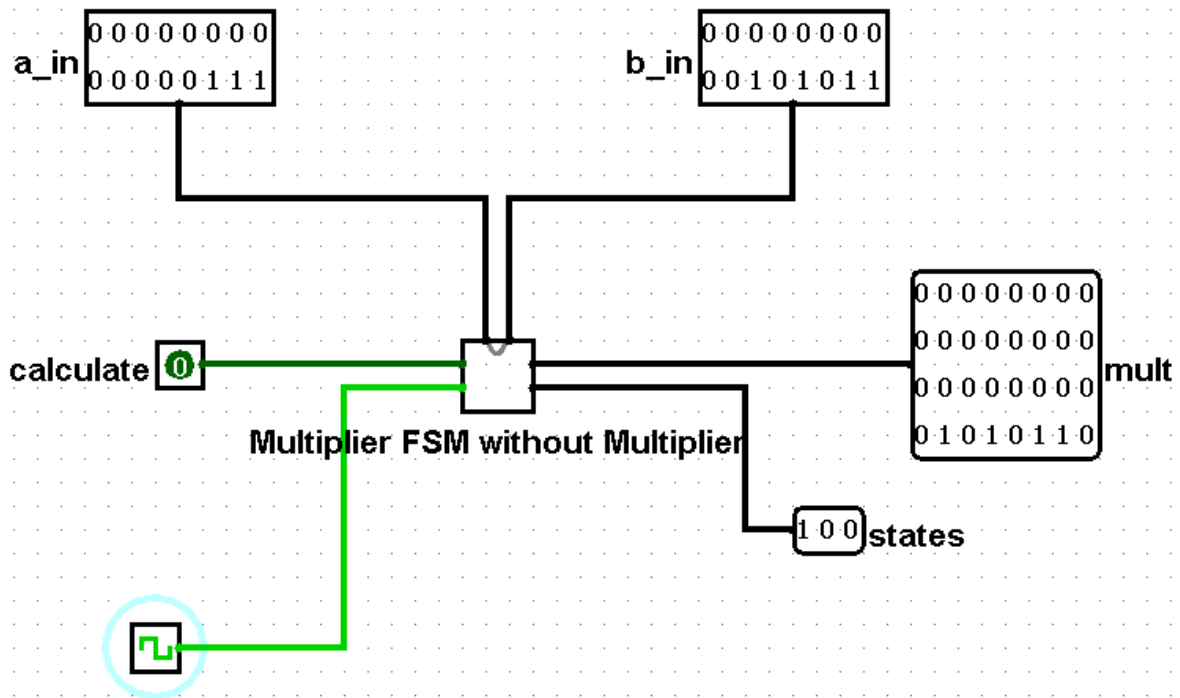

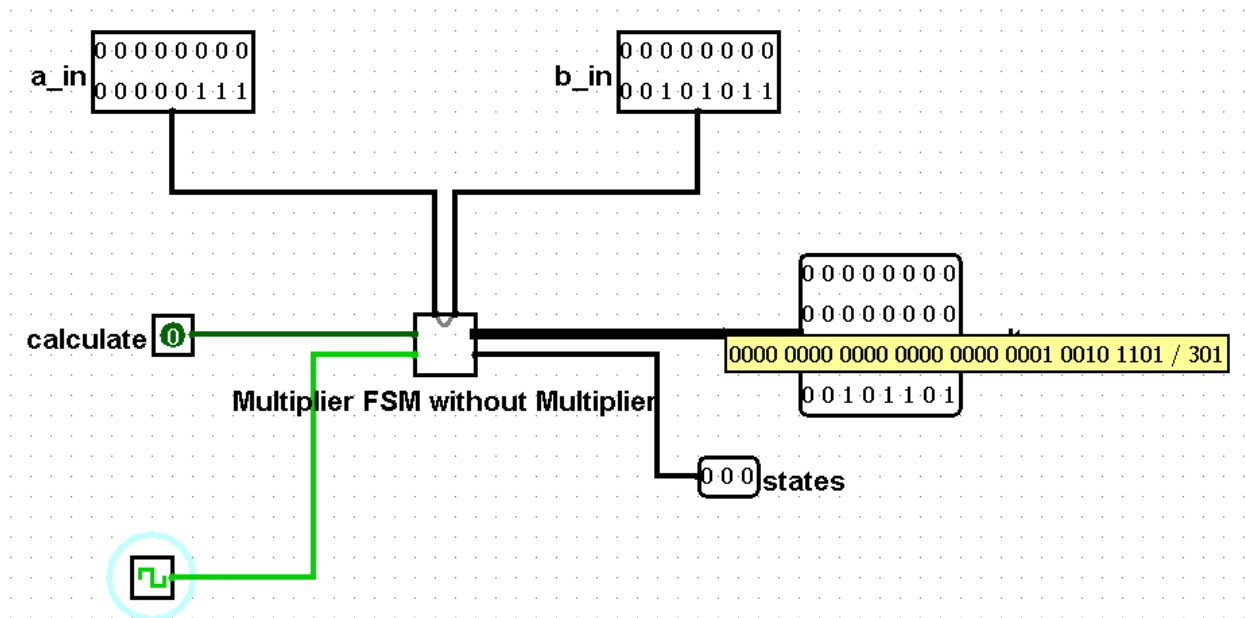- When a_register becomes zero, multiplication will end, and program will go to the start state



- Mult equals to 301. Our simulation successfully ended.